



Πανεπιστήμιο Ιωαννίνων


Ειδικά Θέματα Αρχιτεκτονικής και Προγραμματισμού Μικροεπεξεργαστών

Ενότητα 4: The Processor: Datapath and Control

Διδάσκων: Βαρτζιώτης Φώτιος
Τμήμα Πληροφορικής και Τηλεπικοινωνιών

Implementing MIPS

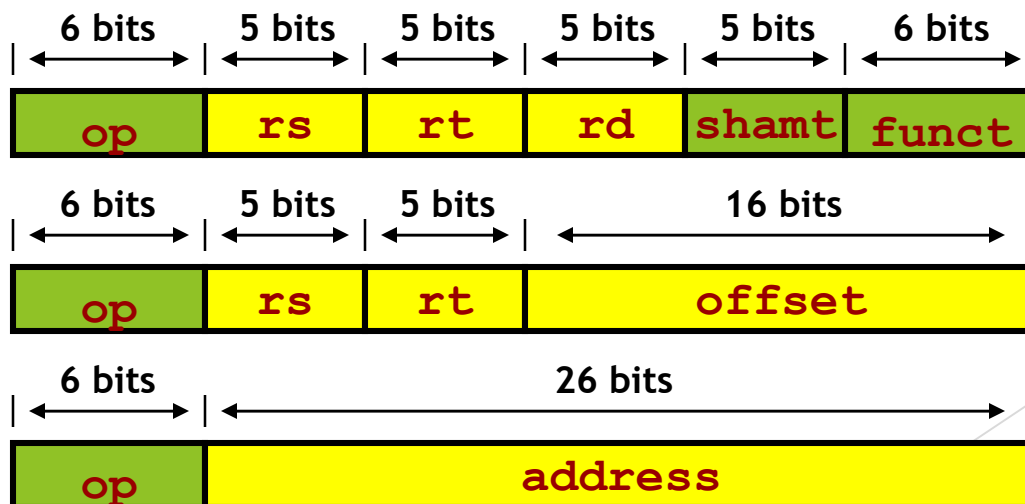- ▶ We're ready to look at an implementation of the MIPS instruction set
- ▶ Simplified to contain only
 - ▶ arithmetic-logic instructions: `add`, `sub`, `and`, `or`, `slt`
 - ▶ memory-reference instructions: `lw`, `sw`
 - ▶ control-flow instructions: `beq`, `j`




R-Format

I-Format

J-Format

Implementing MIPS: the Fetch/Execute Cycle

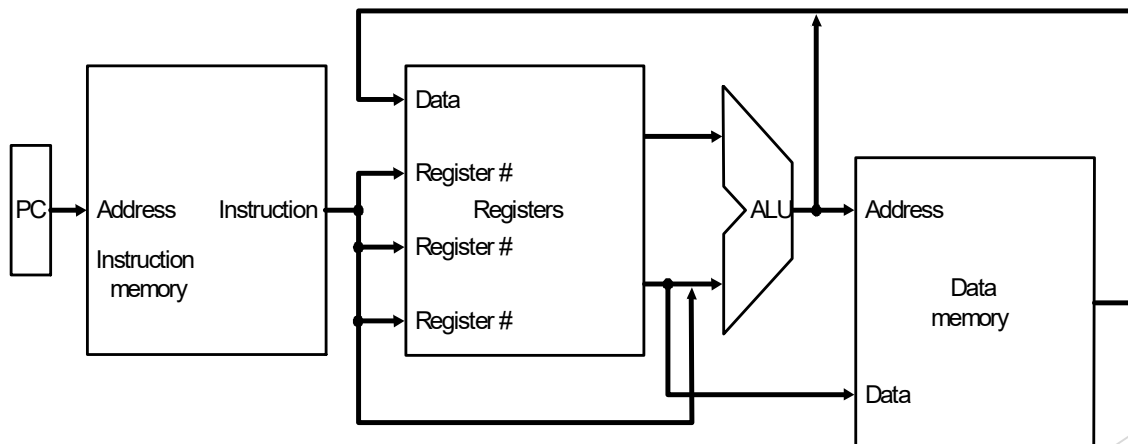- ▶ High-level abstract view of *fetch/execute* implementation
 - ▶ use the program counter (PC) to read instruction address
 - ▶ *fetch* the instruction from memory and increment PC
 - ▶ use fields of the instruction to select registers to read
 - ▶ *execute* depending on the instruction
 - ▶ repeat...



Overview: Processor Implementation Styles

- ▶ Single Cycle
 - ▶ perform each instruction in 1 clock cycle
 - ▶ clock cycle must be long enough for slowest instruction; therefore,
 - ▶ disadvantage: only as fast as slowest instruction
- ▶ Multi-Cycle
 - ▶ break fetch/execute cycle into multiple steps
 - ▶ perform 1 step in each clock cycle
 - ▶ advantage: each instruction uses only as many cycles as it needs
- ▶ Pipelined
 - ▶ execute each instruction in multiple steps
 - ▶ perform 1 step / instruction in each clock cycle
 - ▶ process multiple instructions in parallel - assembly line

Functional Elements




- ▶ Two types of functional elements in the hardware:
 - ▶ elements that *operate on* data (called *combinational elements*)
 - ▶ elements that *contain* data (called *state* or *sequential elements*)

Combinational Elements

- ▶ Works as an *input* \Rightarrow *output function*, e.g., ALU
- ▶ Combinational logic *reads input data from one register and writes output data to another, or same, register*
 - ▶ *read/write happens in a single cycle* - combinational element *cannot store data* from one cycle to a future one



Combinational logic hardware units

   


State Elements

- ▶ State elements contain *data* in internal storage, e.g., *registers* and *memory*
- ▶ All state elements together *define* the *state of the machine*
 - ▶ *What does this mean? Think of shutting down and starting up again...*
- ▶ *Flipflops* and *latches* are 1-bit state elements, equivalently, they are *1-bit memories*
- ▶ The *output(s)* of a flipflop or latch *always* depends on the bit value stored, i.e., its state, and can be called *1/0* or *high/low* or *true/false*
- ▶ The *input* to a flipflop or latch can change its state depending on whether it is clocked or not...

Synchronous Logic: Clocked Latches and Flipflops

 
- ▶ Clocks are used in *synchronous* logic to determine *when* a state element is to be updated
 - ▶ in *level-triggered* clocking methodology either the state changes only when the clock is high or only when it is low (technology-dependent)



- ▶ in *edge-triggered* clocking methodology either the *rising edge* or *falling edge* is active (depending on technology) - i.e., states change only on rising edges or only on falling edge
- ▶ Latches are level-triggered
- ▶ Flipflops are edge-triggered

State Elements on the Datapath: Register File

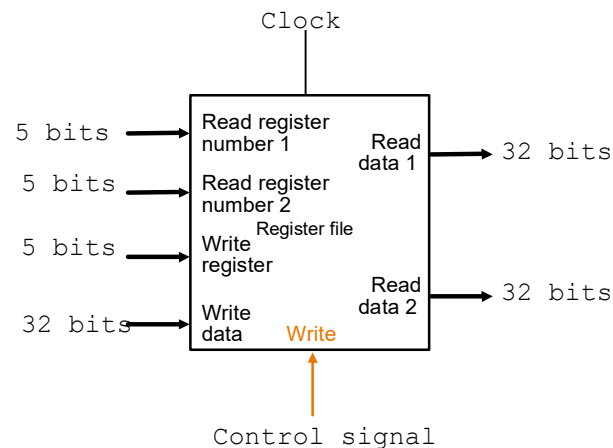
- Registers are implemented with arrays of D-flipflops




Register file with two read ports and one write port

State Elements on the Datapath: Register File

► Port implementation:

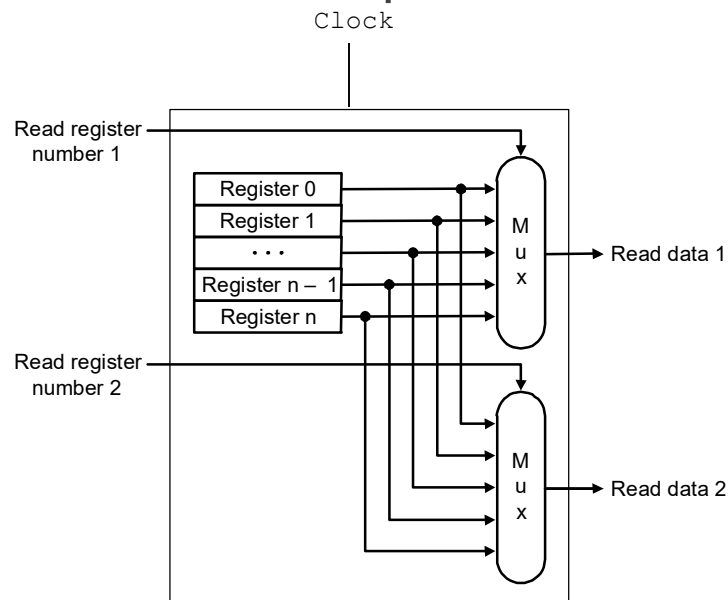

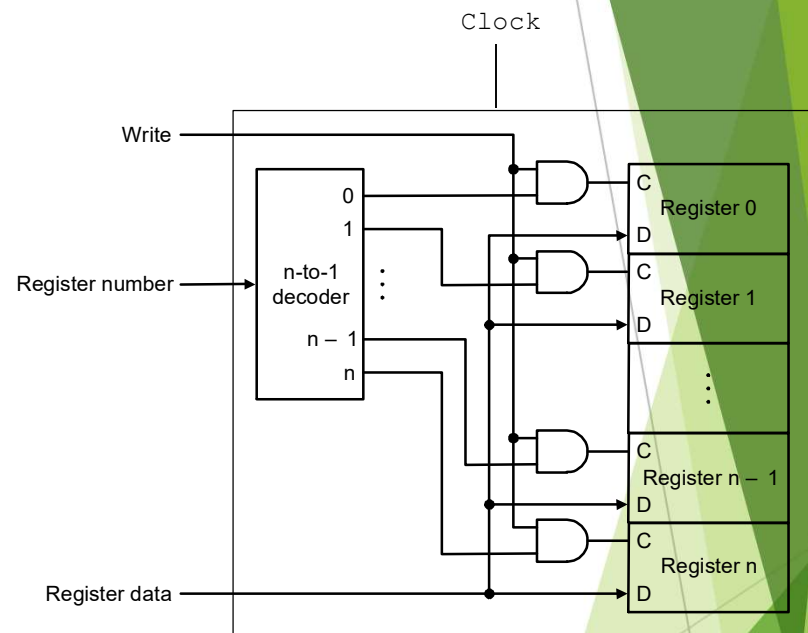Read ports are implemented with a pair of multiplexors – 5 bit multiplexors for 32 registers



Write port is implemented using a decoder – 5-to-32 decoder for 32 registers. Clock is relevant to write as register state may change only at clock edge


VHDL

- ▶ All components that we have discussed - and shall discuss - can be fabricated using VHDL (or other HDL)
- ▶ Refer to VLSI design slides and examples


Single-cycle Implementation of MIPS

- ▶ Our first implementation of MIPS will use a *single* long clock cycle for every instruction
- ▶ Every instruction begins on one up (or, down) clock edge and ends on the next up (or, down) clock edge
- ▶ This approach is *not practical* as it is much slower than a *multicycle* implementation where different instruction classes can take different numbers of cycles
 - ▶ in a single-cycle implementation every instruction must take the same amount of time as the slowest instruction
 - ▶ in a multicycle implementation this problem is avoided by allowing quicker instructions to use fewer cycles
- ▶ Even though the single-cycle approach is not practical it is simple and useful to understand first
- ▶ *Note* : we shall implement `jump` at the very end

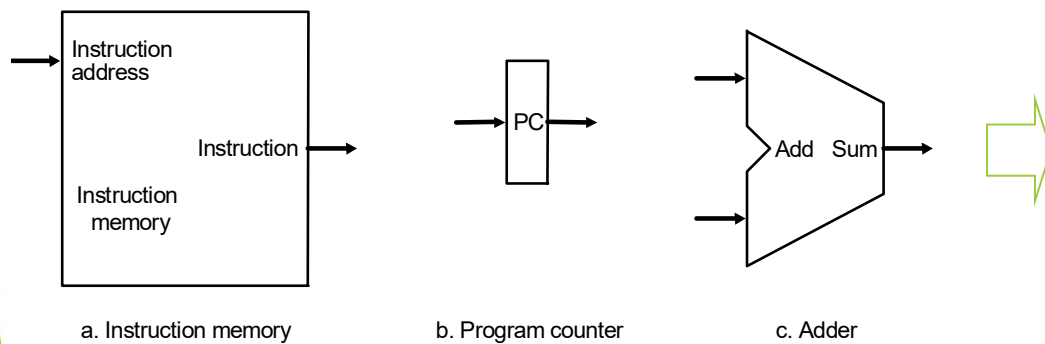Datapath: Instruction Store/Fetch & PC Increment




 Three elements used to store and fetch instructions and increment the PC




Datapath


Animating the Datapath

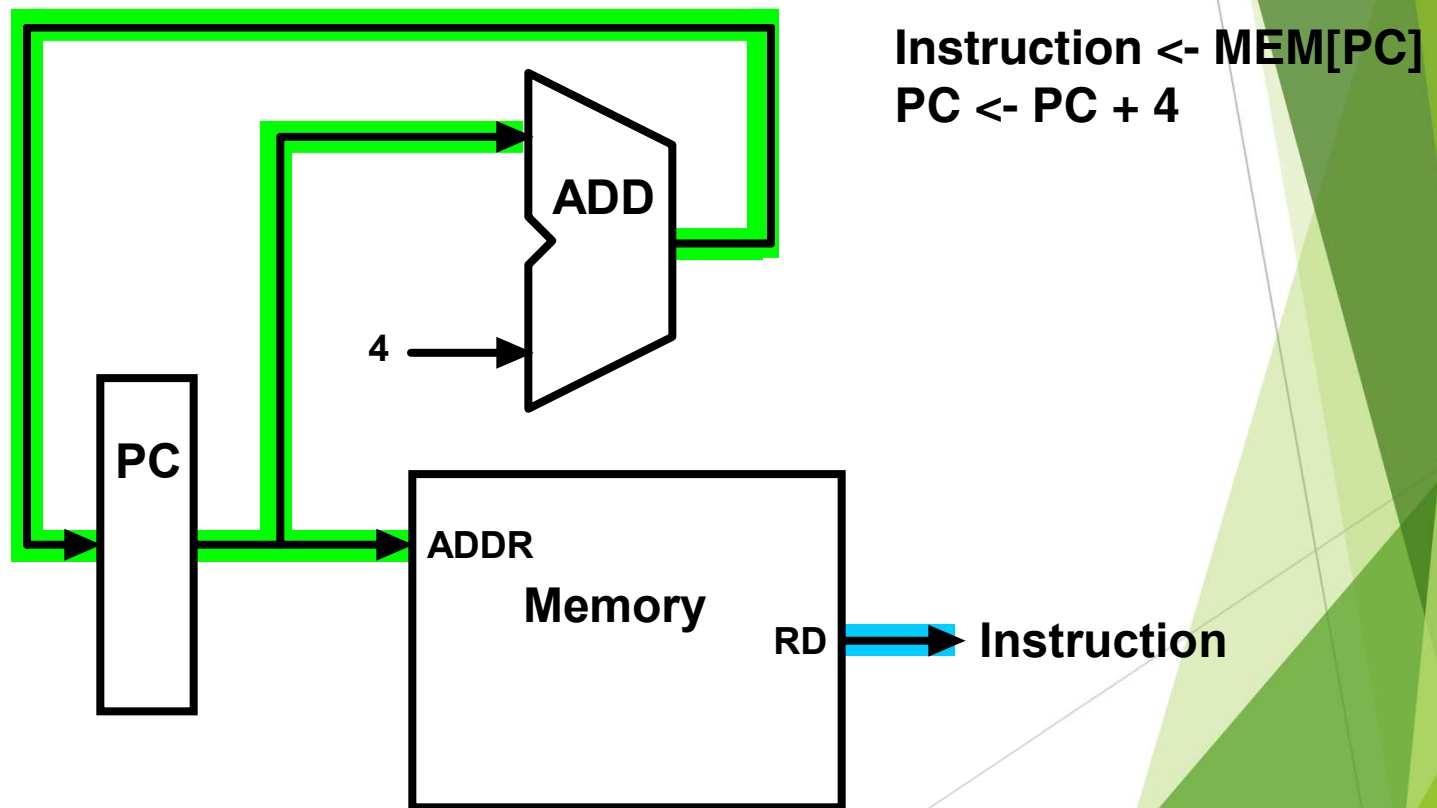


Datapath: R-Type Instruction

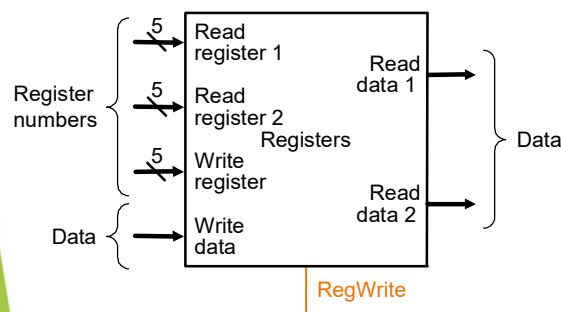

a. Registers

 

b. ALU

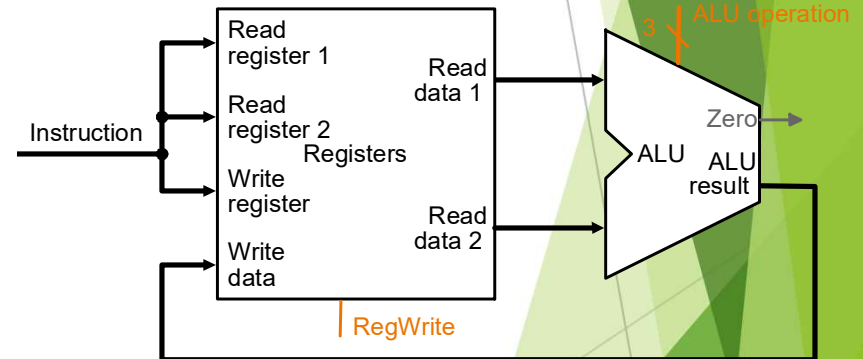

Datapath

Two elements used to implement R-type instructions


Animating the Datapath

Instruction




add rd, rs, rt

$R[rd] \leftarrow R[rs] + R[rt];$

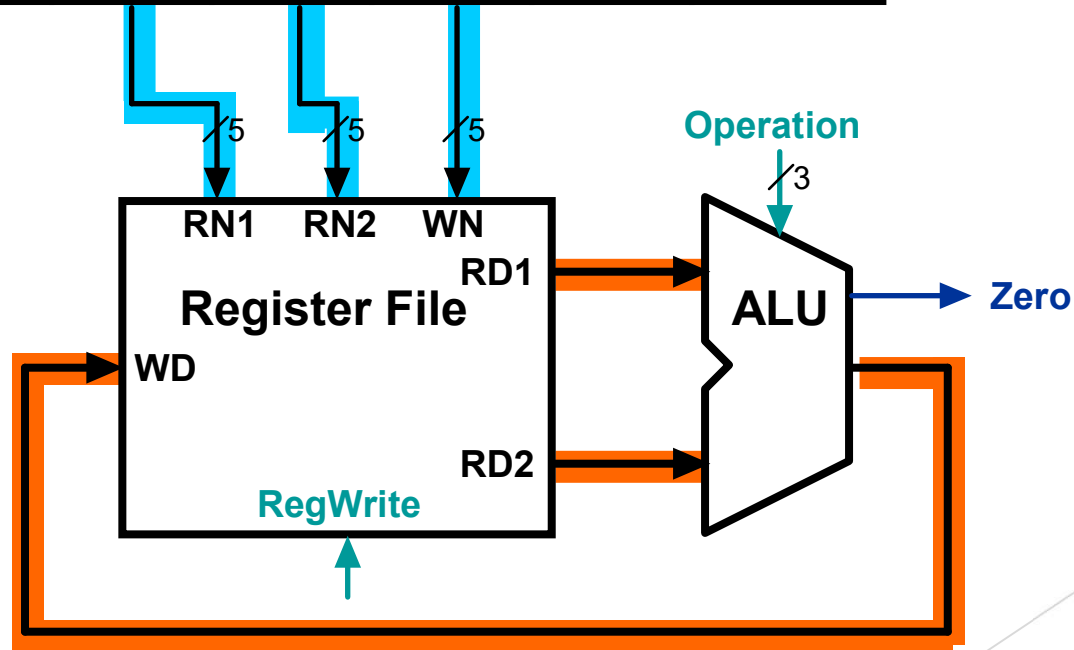

Datapath: Load/Store Instruction

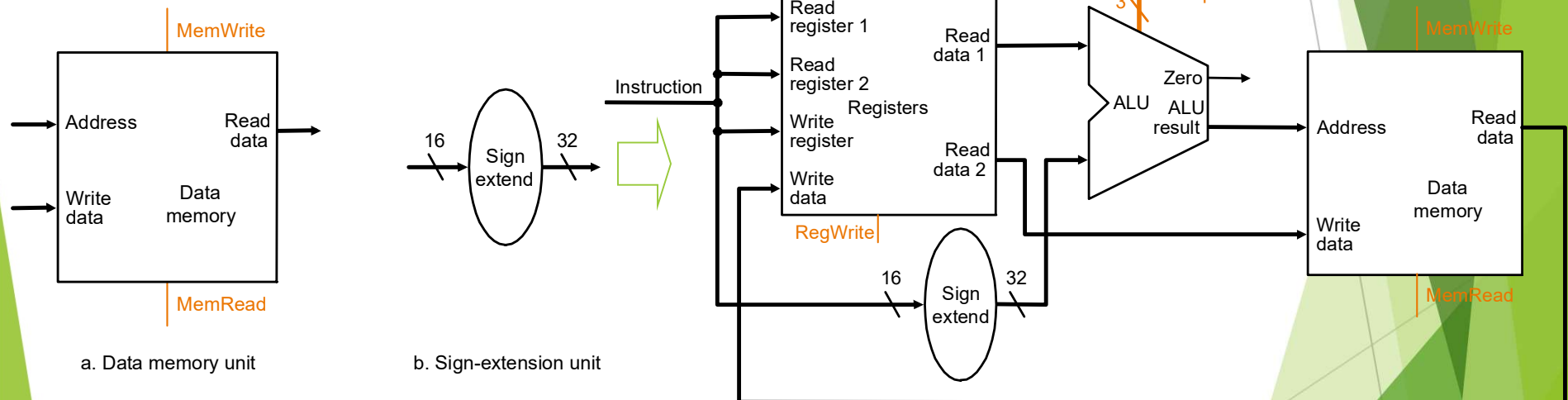


**Two additional elements used
To implement load/stores**

Datapath


Animating the Datapath

`lw rt, offset(rs)`

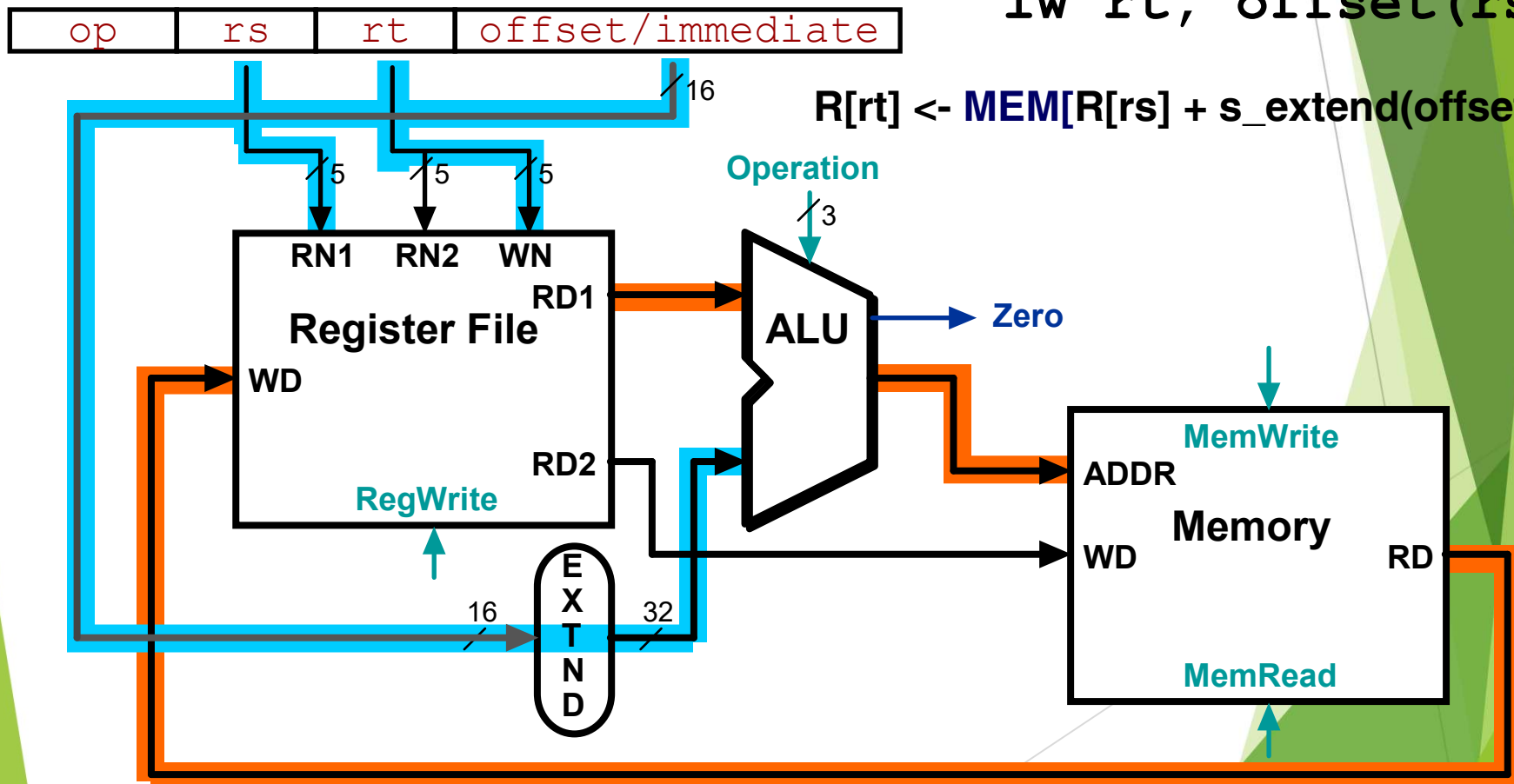$R[rt] \leftarrow \text{MEM}[R[rs] + \text{s_extend}(\text{offset})];$




Animating the Datapath

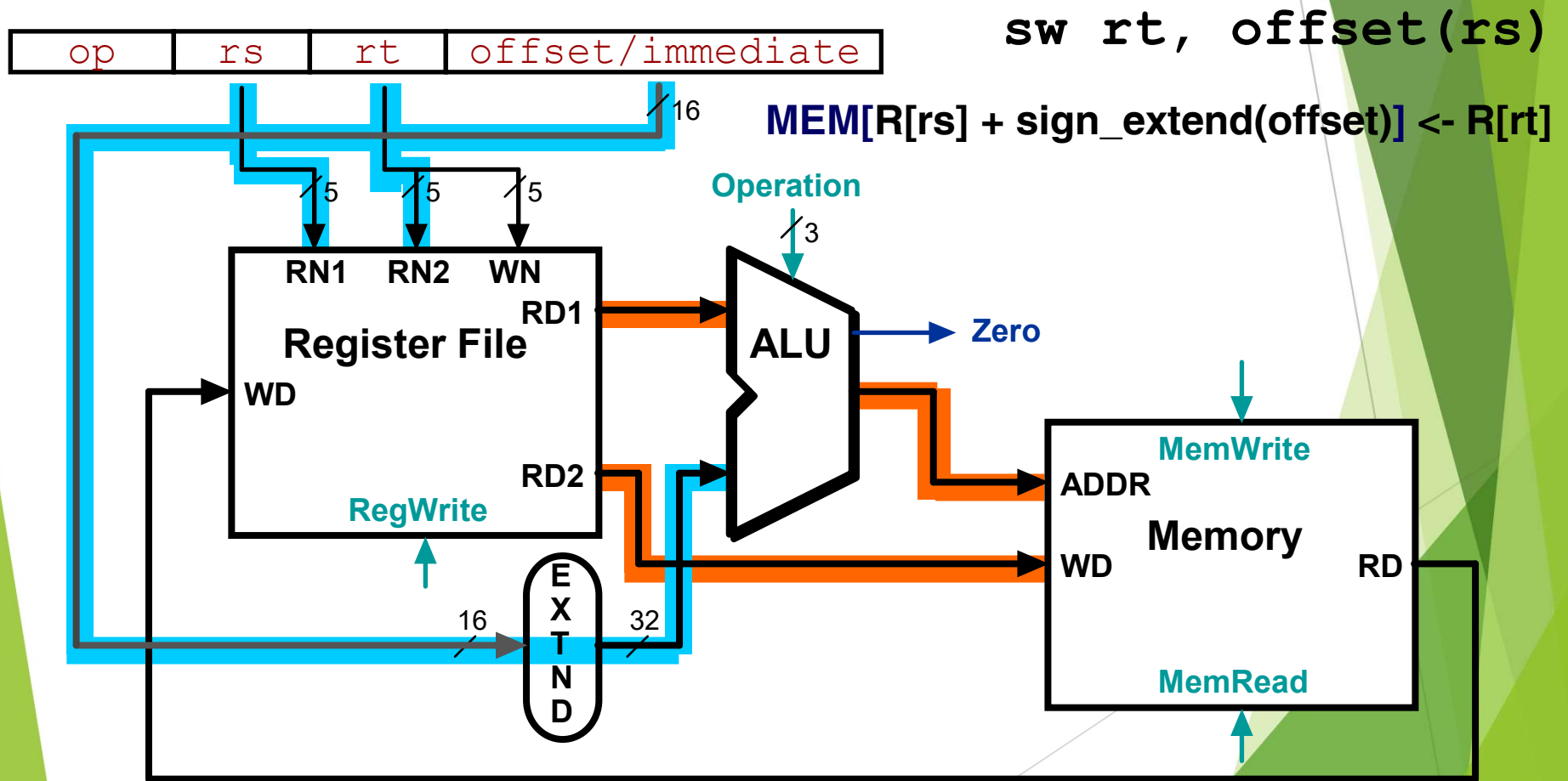


Datapath: Branch Instruction

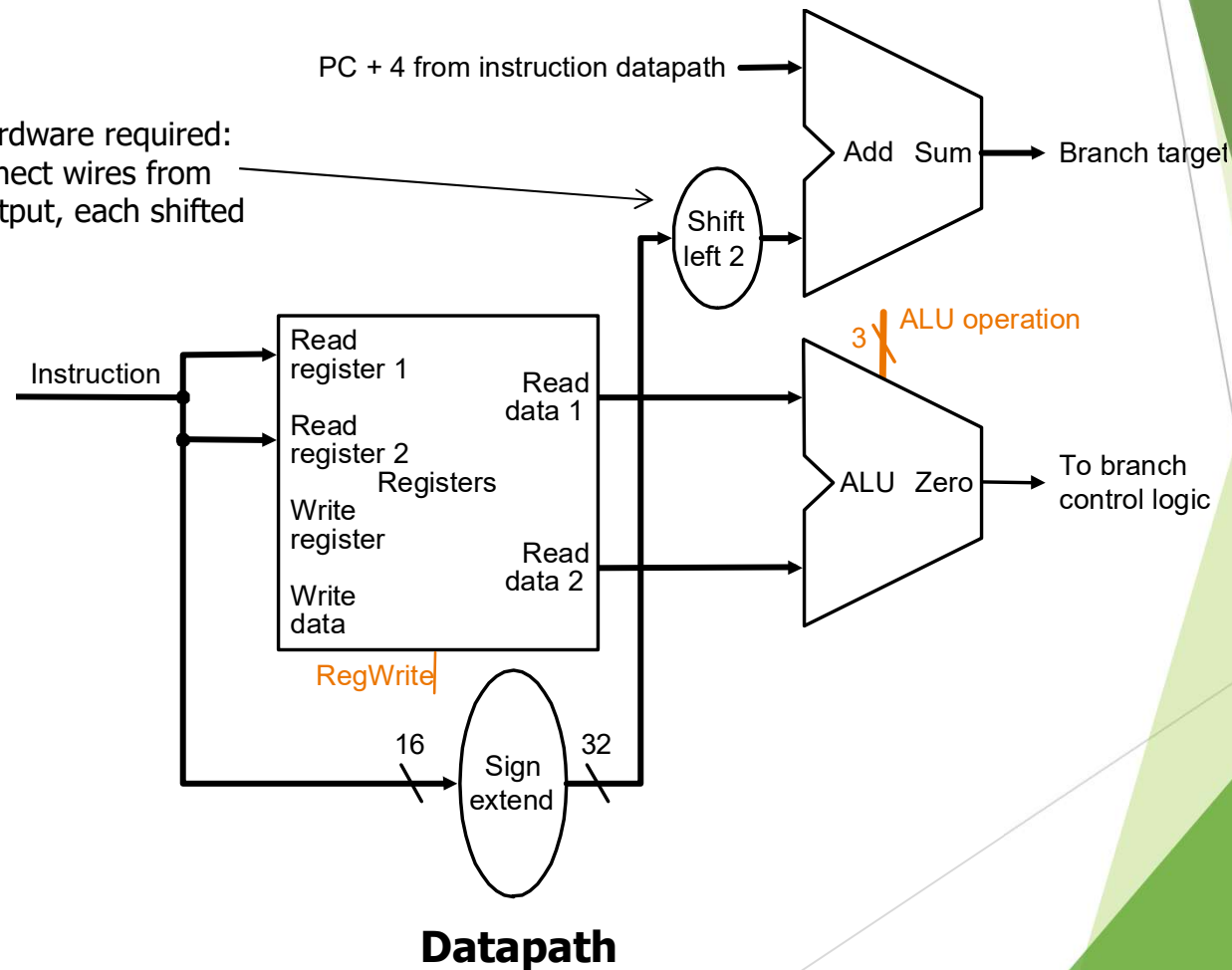No shift hardware required:
simply connect wires from
input to output, each shifted
left 2 bits




Animating the Datapath

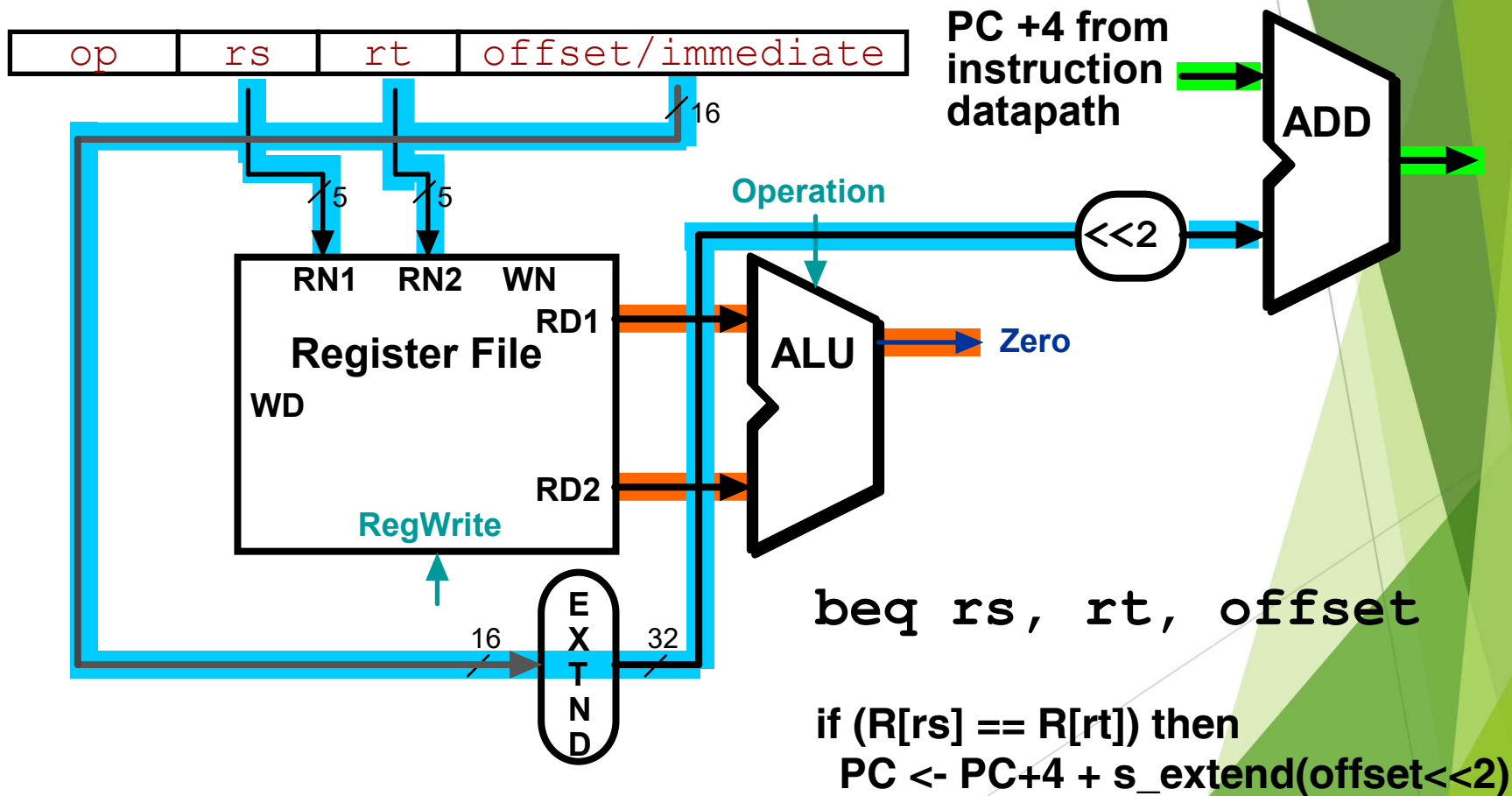

MIPS Datapath I: Single-Cycle

Combining the datapaths for R-type instructions and load/stores using two multiplexors

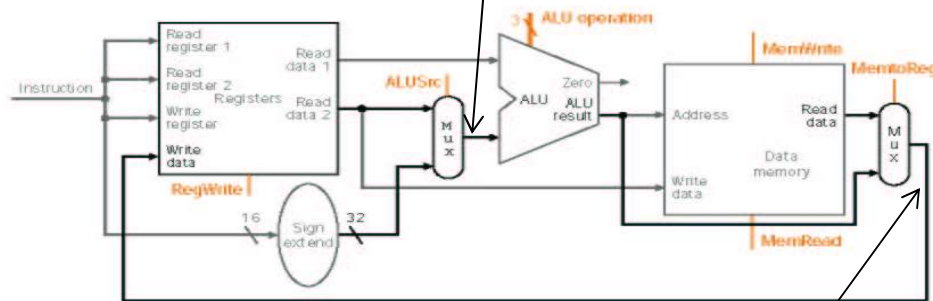
Input is either register (R-type) or sign-extended lower half of instruction (load/store)



Data is either from ALU (R-type) or memory (load)


Animating the Datapath: R-type Instruction

add rd,rs,rt

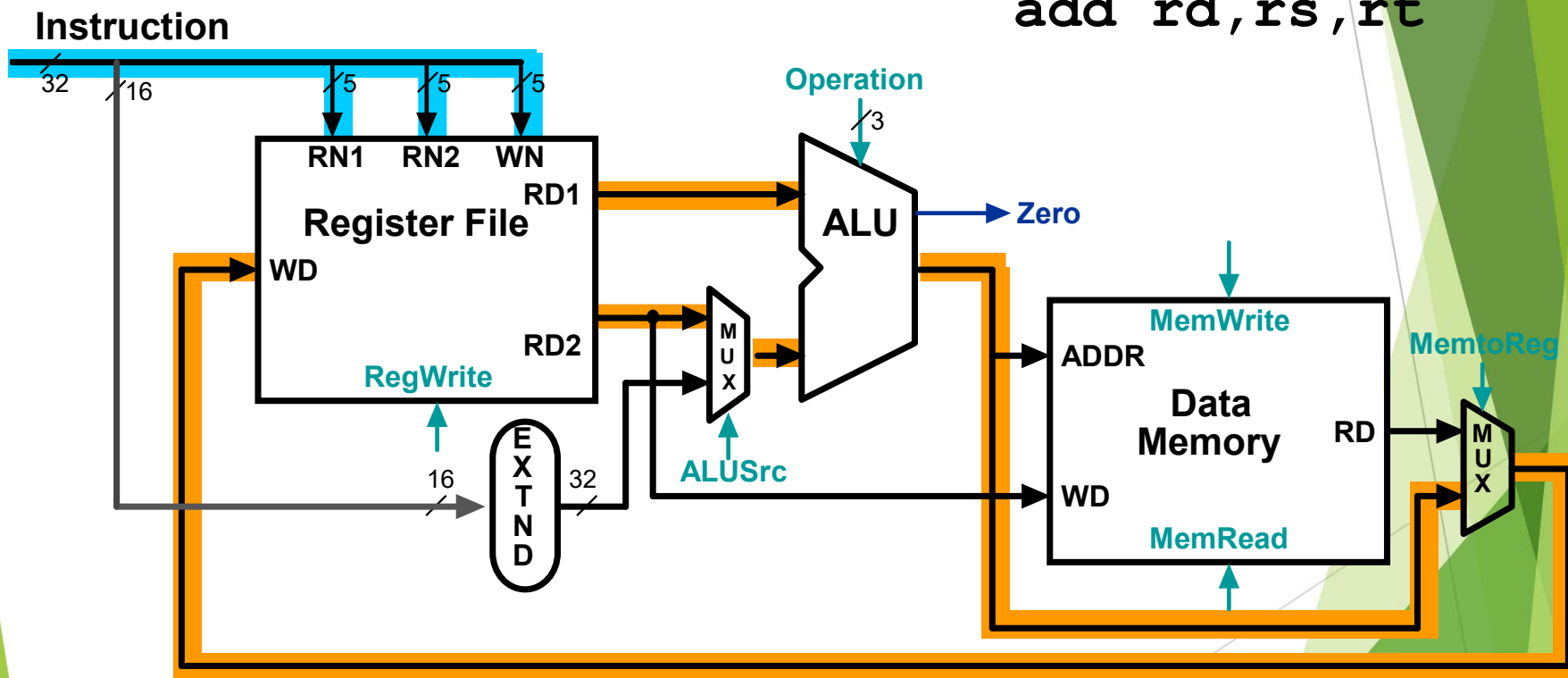


Animating the Datapath: Load Instruction


`lw rt,offset(rs)`

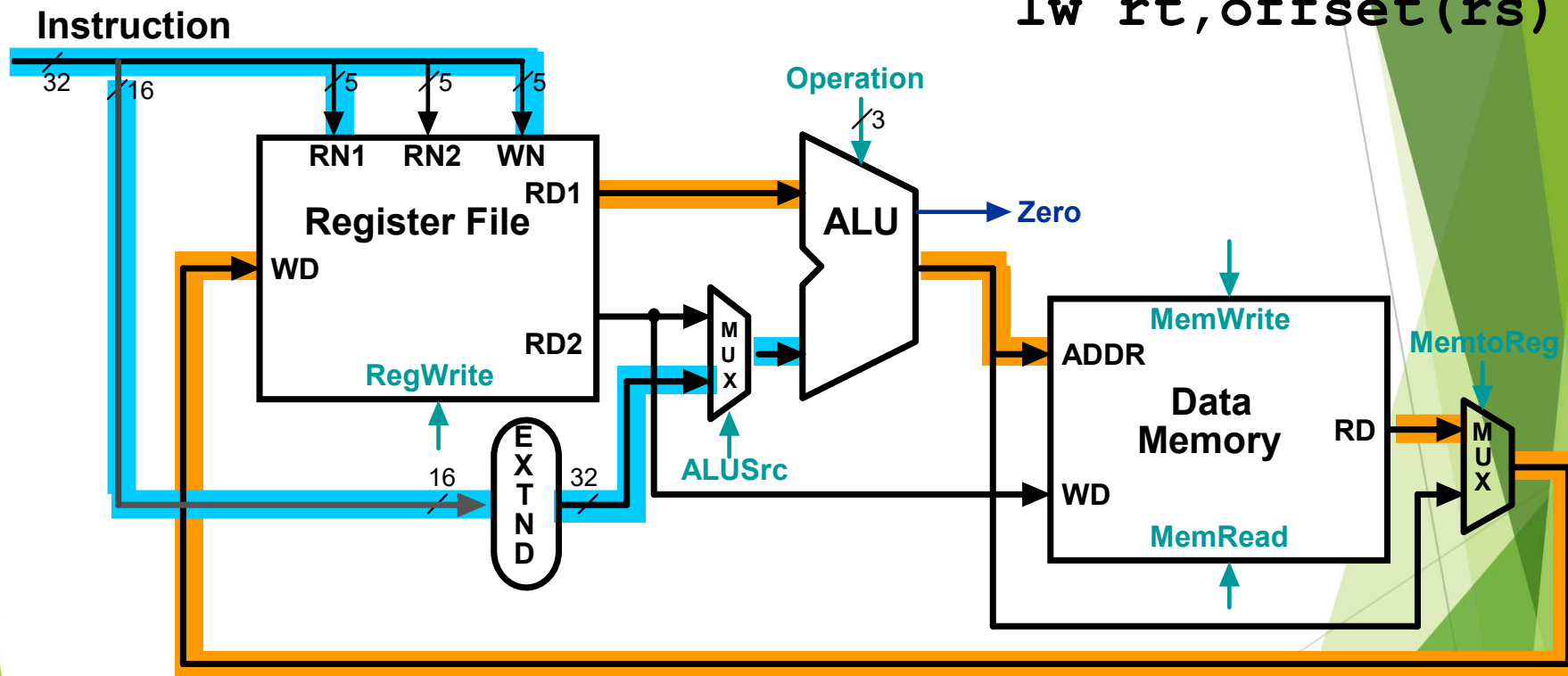

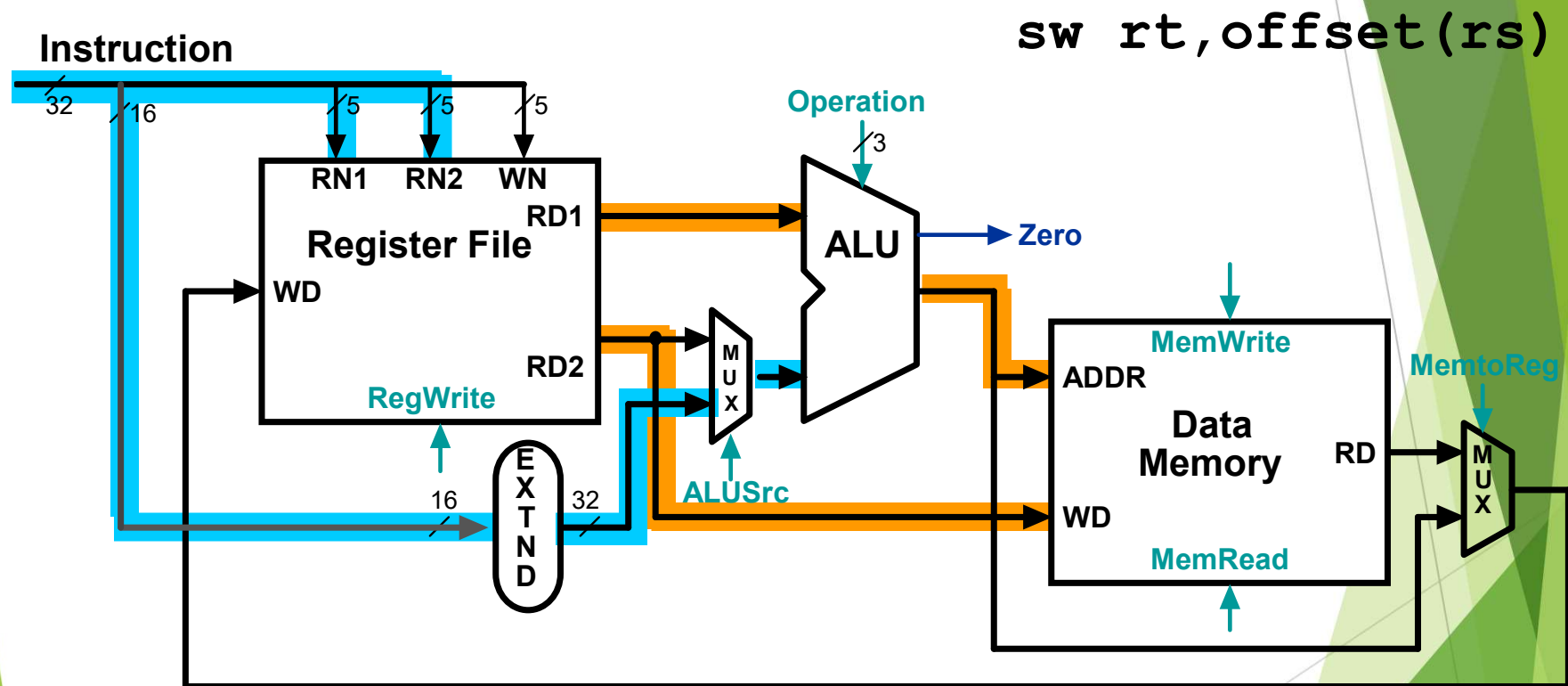
Animating the Datapath: Store Instruction



MIPS Datapath II: Single-Cycle

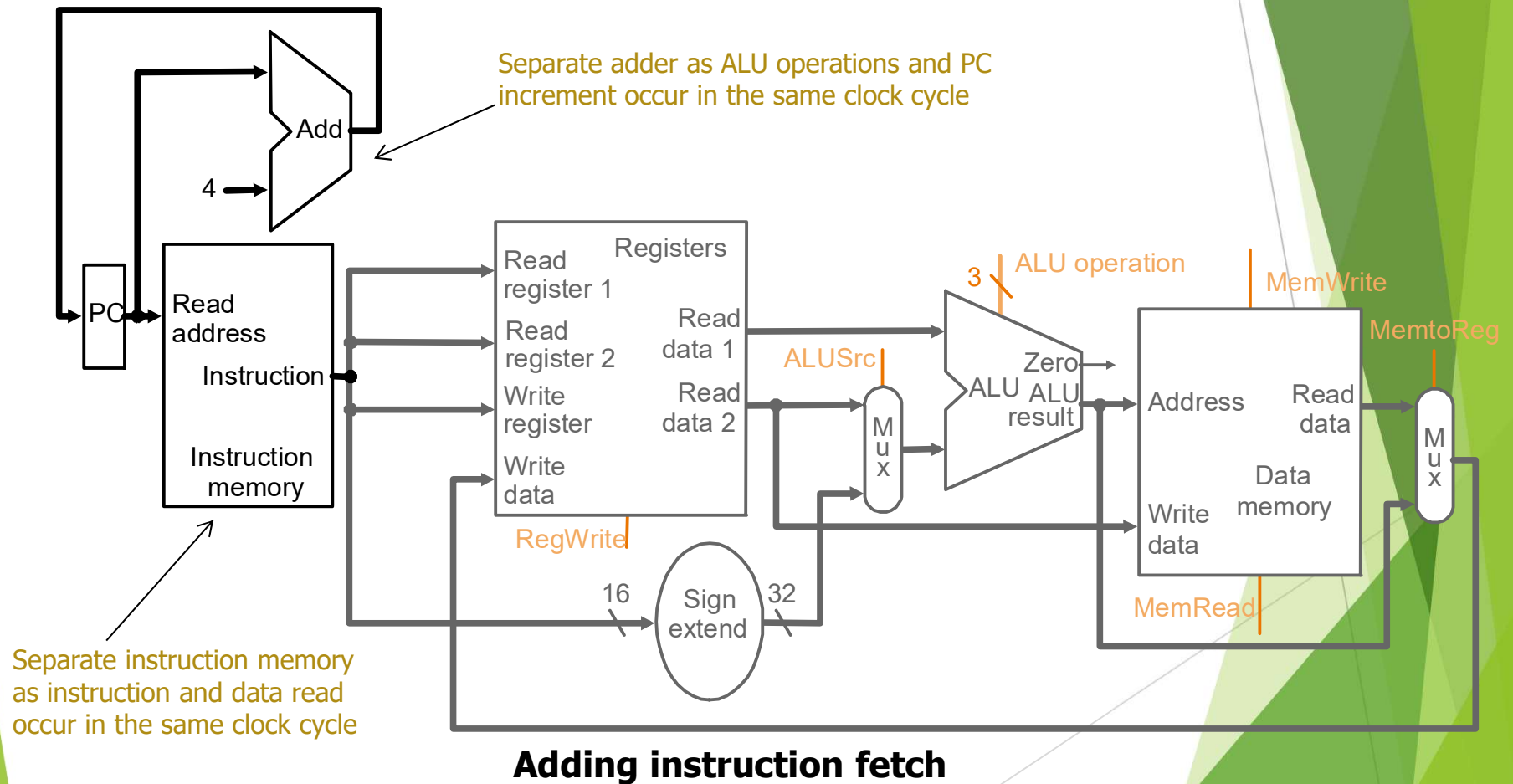

MIPS Datapath III: Single-Cycle

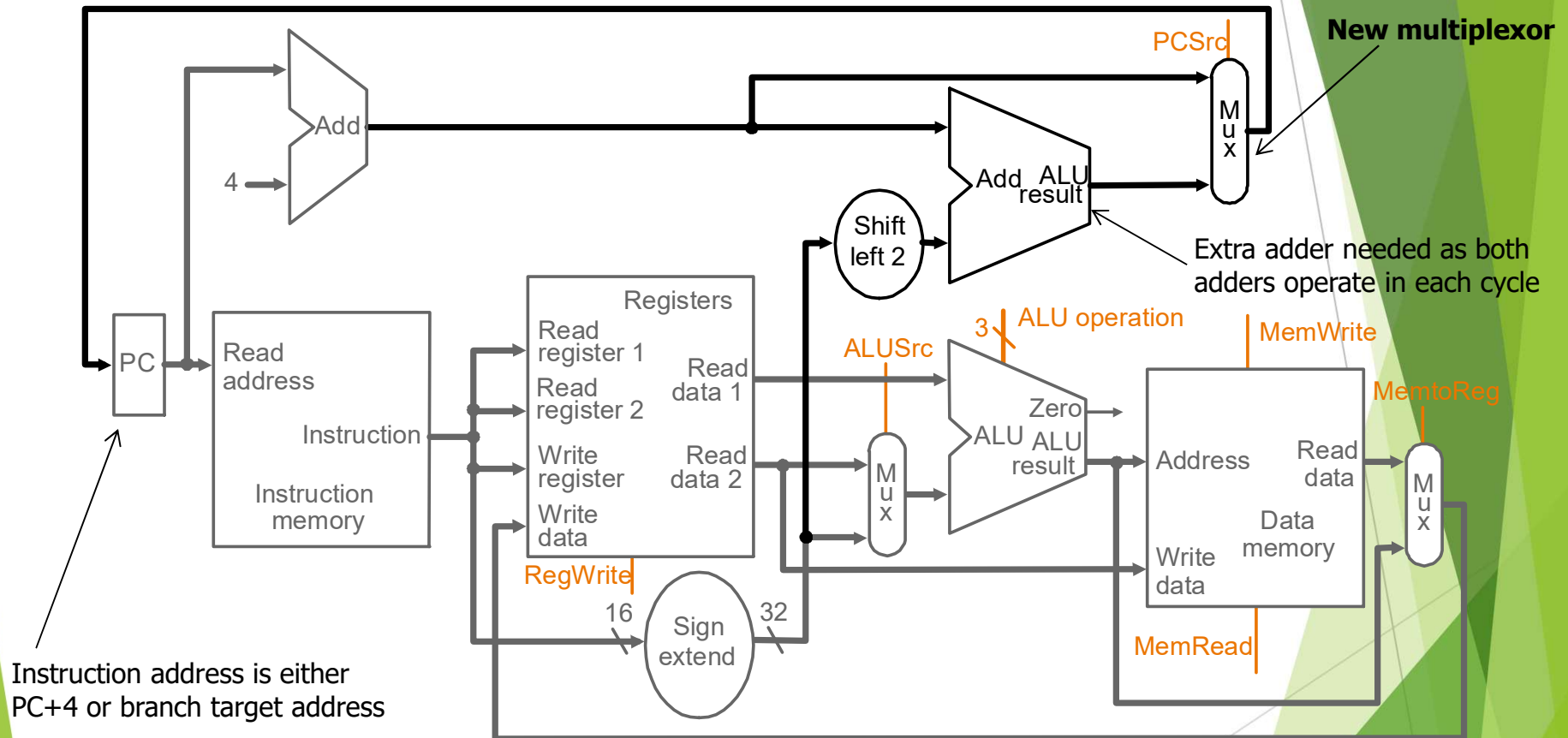


Adding branch capability and another multiplexor


Important note: in a single-cycle implementation data cannot be stored during an instruction – it only moves through combinational logic

Question: is the MemRead signal really needed?! Think of RegWrite...!


Datapath Executing add

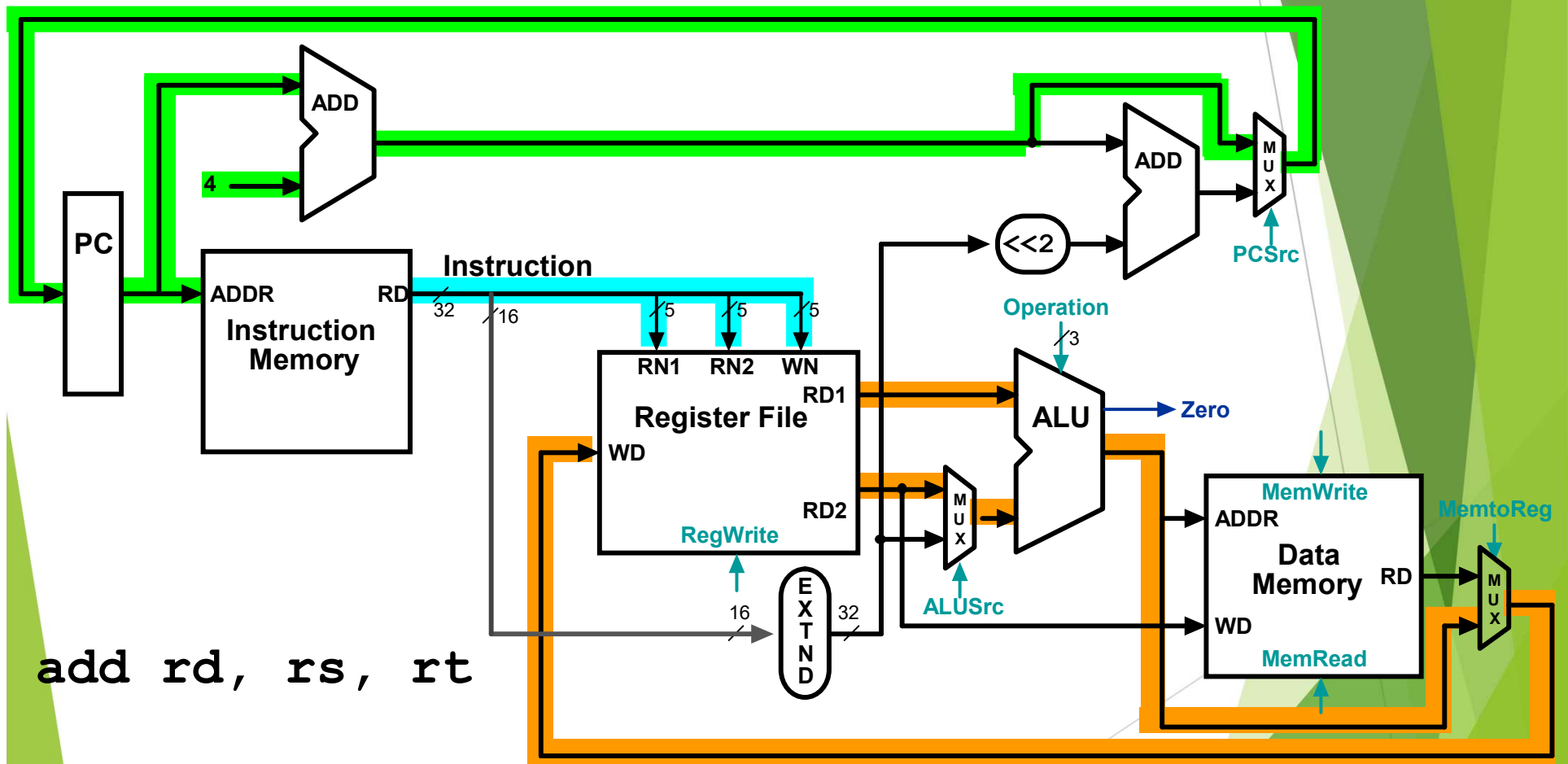

Datapath Executing lw

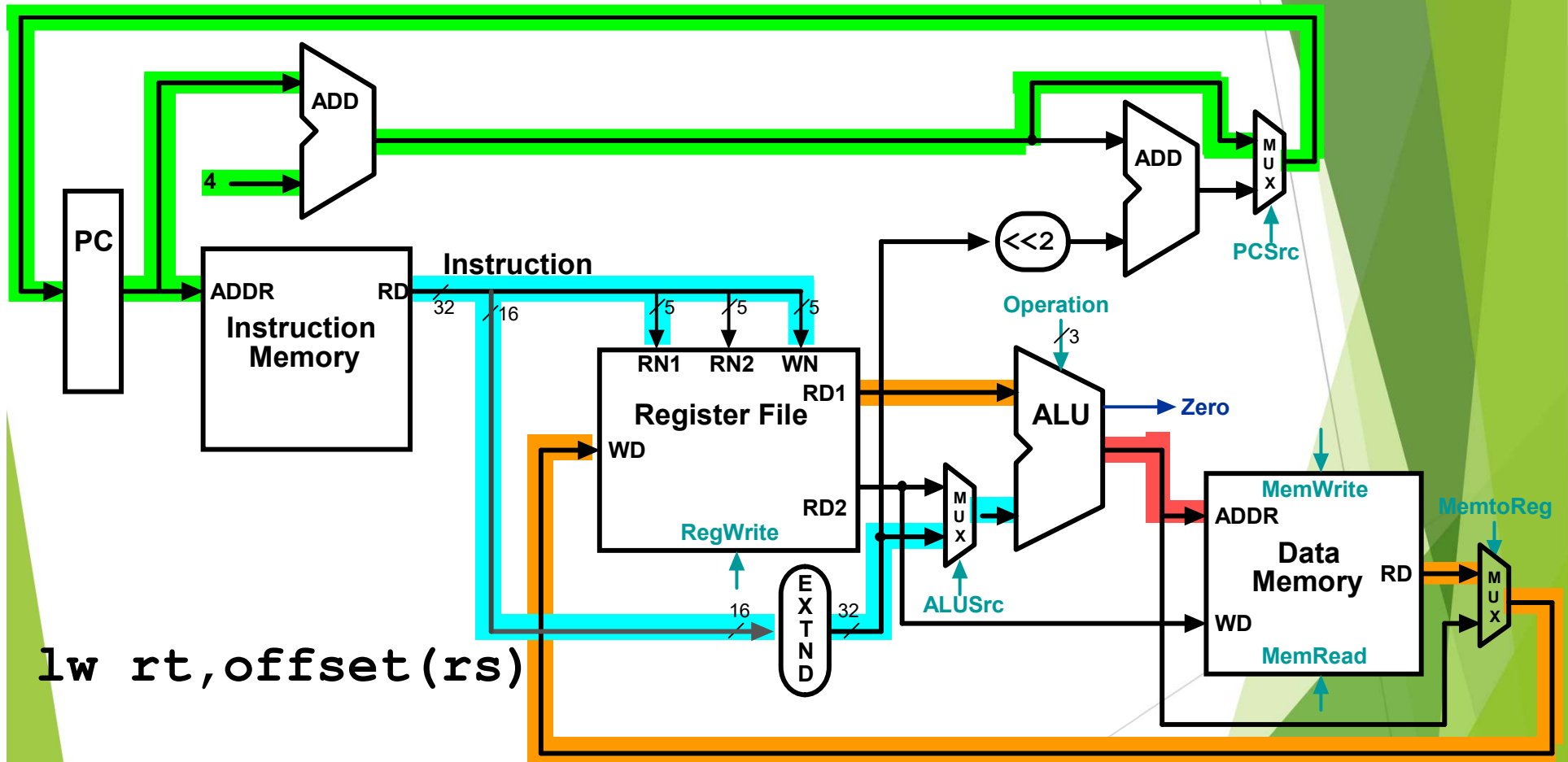

Datapath Executing sw

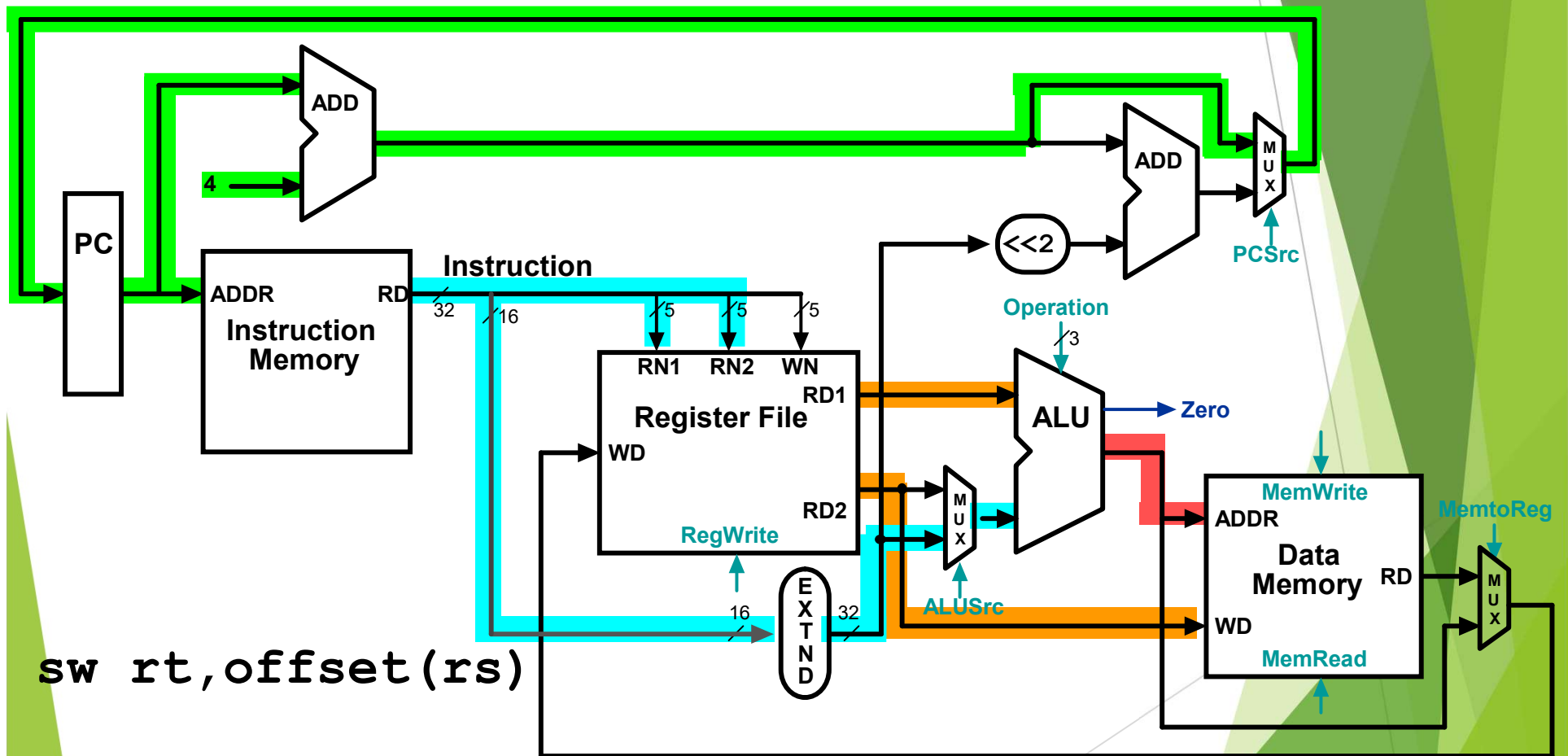

Datapath Executing beq

